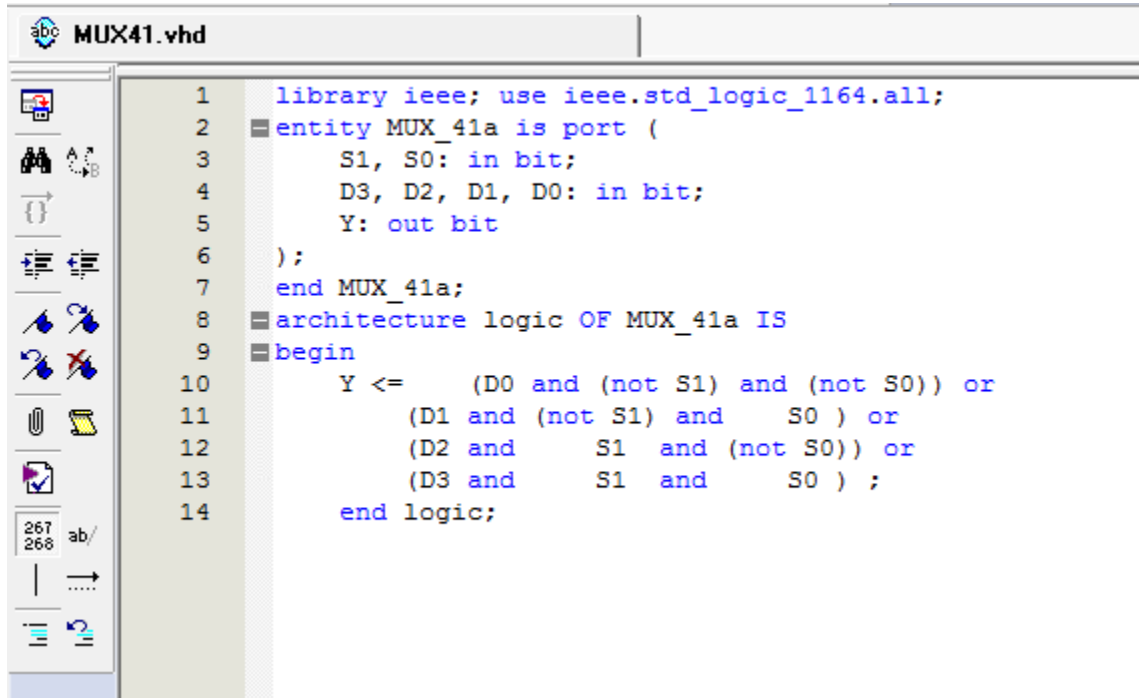


Lab 6 Summary
Irvin, Mitchell
Section 7441
3/11/16


Prelab Part 1: VHDL of a 41MUX




```
1  library ieee; use ieee.std_logic_1164.all;
2  entity MUX_41a is port (
3      S1, S0: in bit;
4      D3, D2, D1, D0: in bit;
5      Y: out bit
6  );
7  end MUX_41a;
8  architecture logic OF MUX_41a IS
9  begin
10     Y <= (D0 and (not S1) and (not S0)) or
11         (D1 and (not S1) and S0 ) or
12         (D2 and S1 and (not S0)) or
13         (D3 and S1 and S0 ) ;
14 end logic;
```

Verify that it works: if it didn't work the rest of my lab wouldn't work. I compiled it and created a VWF file to test it but that entire project folder got corrupted and I had to redo everything so please just let the rest of my lab be proof that it works

Part 2: ALU Design Inputs/Outputs

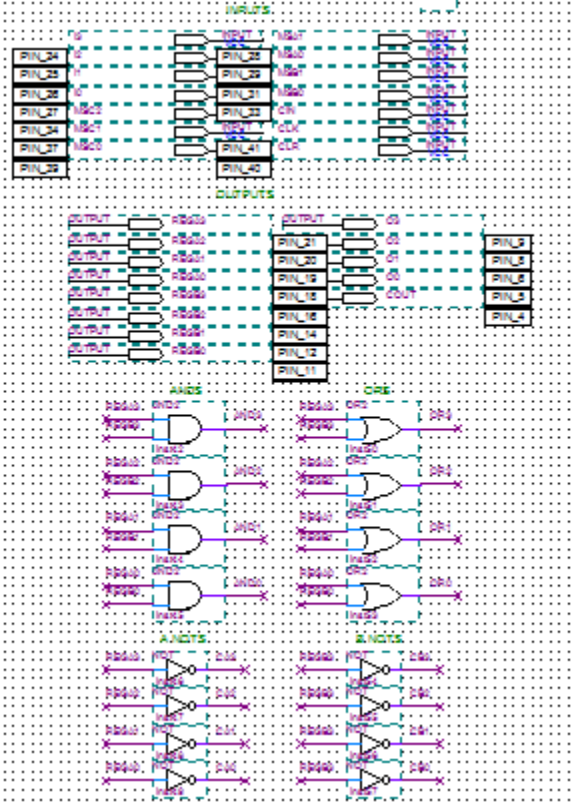

Logic Design

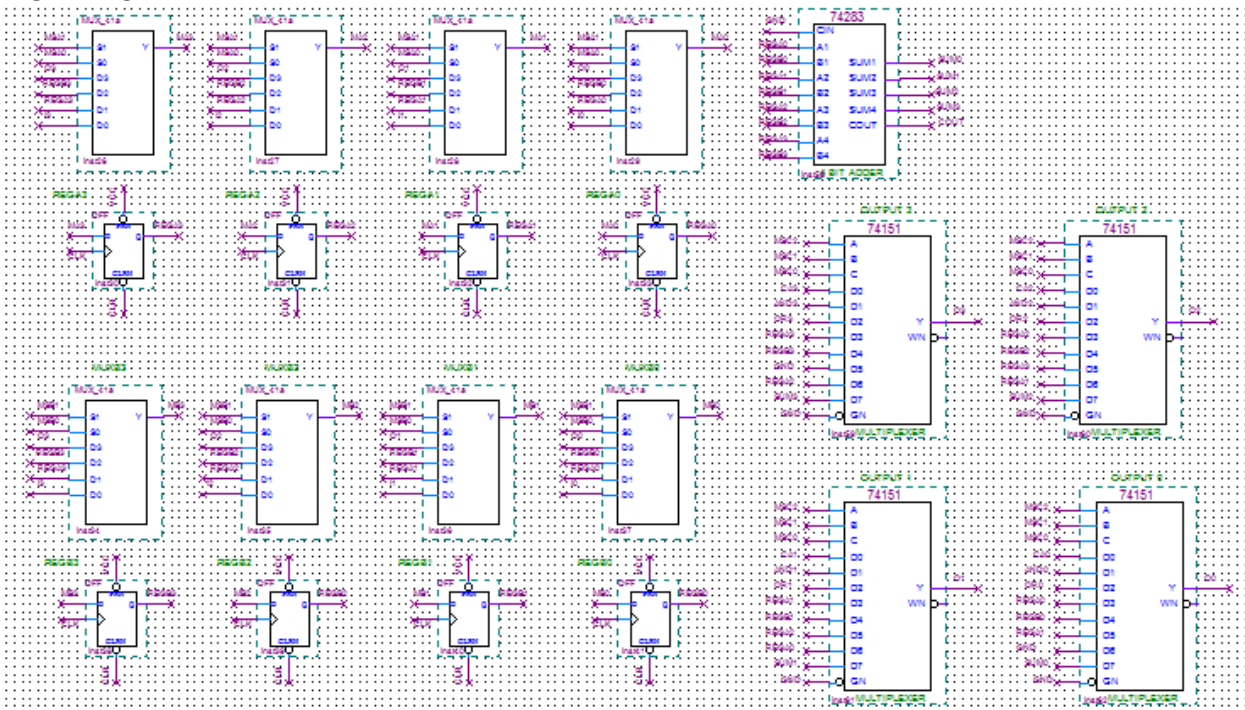

Part 3: Simple Program Design

Lab 6

Part 3:

1. write simple programs for

a) 1. $I3:0 = 1001$

$MSA = 00$ $MSC = XXX$

$MSB = XX$

$\uparrow \int$, $A = 1001$ (9)

2. $MSA = 01$ $MSC = 000$

$MSB = 11$

$\uparrow \int$, $B = 0110$ (6)

b) 1. $I3:0 = 1011$, $A = 11_{10}$

$MSA = 00$ $MSC = XXX$

$MSB = XX$

$\uparrow \int$, $A = 1011$

2. $I3:0 = 0110$, $B = 6$

$MSA = 01$ $MSC = XXX$

$MSB = 00$

$\uparrow \int$, $A = 1011$, $B = 0110$

$A = A + B$, $B = B$

3. $MSA = 11$ $MSC = 111$

$MSB = 10$

$\uparrow \int$, $A = 0001$, $COUT = 1$, $B = 0110$

$\begin{array}{r} 011 \\ 011 \\ \hline 0001 \end{array}$

c) ① $A = \overset{11}{\cancel{111111}}, B = \overset{6}{\cancel{111111}}$

$I3:0 = 1011$

$MSA = 00 \quad MSC = XXX$

$MSB = XX$

$\uparrow \sqrt{\quad}, A = 1011$

$B = 6$

② $I3:0 = 0110$

$MSA = 01 \quad MSC = XXX$

$MSB = 00$

$\uparrow \sqrt{\quad}, A = 1011, B = 0110$

③ $\cancel{A \cdot B} B = A \cdot B, A = A$

$MSA = 01 \quad MSC = 001$

$MSB = 11$

$\uparrow \sqrt{\quad}, A = 1011, B = 0010$

d) REPEAT ① and ② from part a) \rightarrow

$\therefore A = 1011, B = 0110$

① $MSA = 11 \quad MSC = 110$

$MSB = 10$

$\uparrow \sqrt{\quad}, A = 1111, B = 0110$

e) ① $A = 9$

$I3:0 = 1001$

$MSA = 00 \quad MSC = XXX$

$MSB = XX$

$A \uparrow \sqrt{\quad}, A = 1001$

② shift left, store in B

$MSA = 01 \quad MSC = 110$

$MSB = 11$

$\uparrow \sqrt{\quad}, A = 1001, B = 0010$

f) ① $A = 3$

$I3:0 = 0011$

$MSA = 00$ $MSC = XXX$

$MSB = XX$

↑ \int , $A = 0011$

② $A = 4$, load 2 into B

$I3:0 = 0010$

$MSA = 11$ $MSC = 110$

$MSB = 00$

↑ \int , $A = 0110$, $B = 0010$

③ second shift for A

$MSA = 11$ $MSC = 110$

$MSB = 10$

↑ \int , $A = 1100$, $B = 0010$

④ Add 2 to A

$MSA = 11$ $MSC = \overset{111}{\cancel{110}}$

$MSB = 10$

↑ \int , $A = 1110$, $B = 0010$

⑤ Divide by 4

$MSA = 11$ $MSC = 101$

$MSB = \cancel{11}XX$

↑ \int , $A = 0111$, ~~$B = 0010$~~

⑥ $MSA = 11$ $MSC = 101$

$MSB = XX$

↑ \int , $A = 0011$,

Verification of Prelab Part 3 in Quartus

